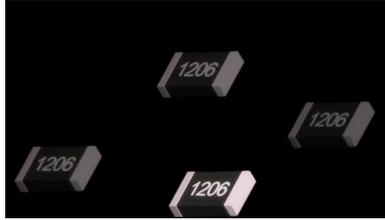


MOS- Controlled Thyristor (MCT)

Author john


1.



2. 1. Now Playing

Up Next *what are SMD Resistors and their Role in Smartphone Technology !*

5:02

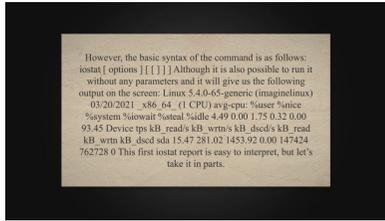


2. Now Playing

Up Next *How to use iostat command in Linux explained with examples*

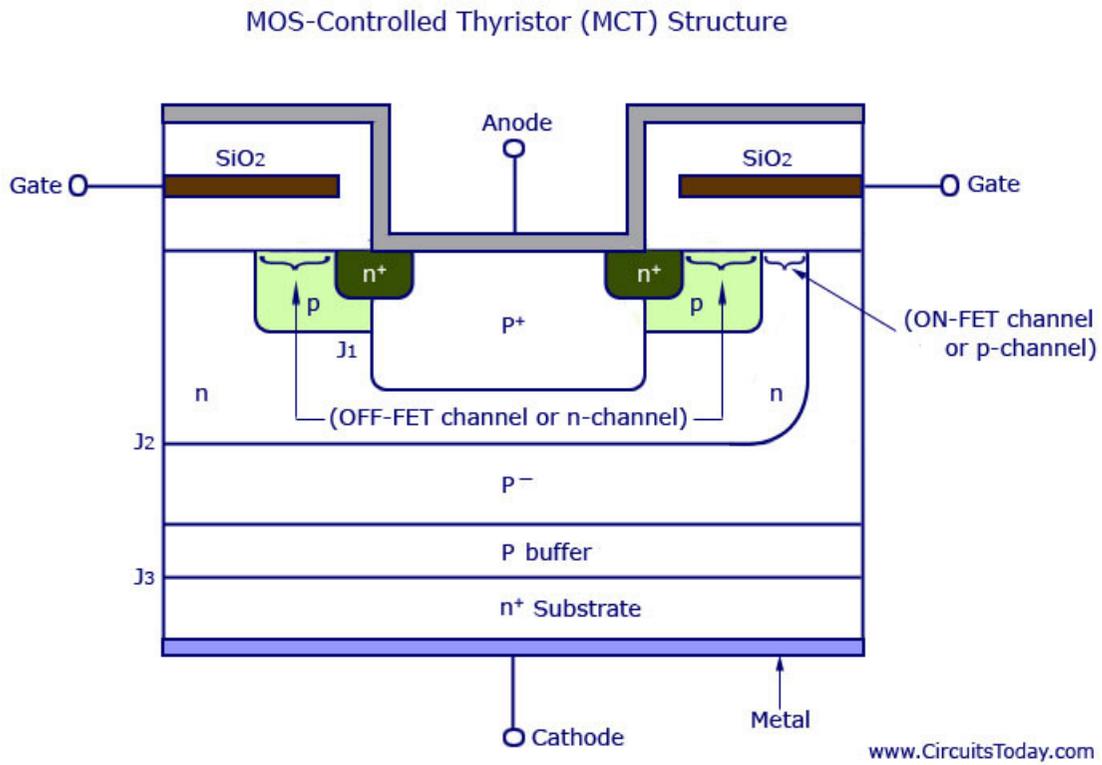4:37

Out of many semiconductor controlled devices, MCT is considered to be the latest. The device is basically a thyristor with two MOSFET's built into the gate structure. A **MOSFET** is used for turning ON the MCT and another one is used for turning it OFF. The device is mostly used for switching applications and has other characteristics like high frequency, high power, and low conduction drop and so on. An MCT combines the feature of both conventional four layer **thyristor** having regenerative action and MOS- gate structure. In this device, all the gate signals are applied with respect to anode, which is kept as the reference. In a normally used **SCR**, cathode is kept as the reference terminal for gate signals.

The basic structure of an MCT cell is shown in the figure below.




MOS Controlled Thyristor (MCT) Structure

⊗ In practice, a MCT will include thousands of these basic cells connected in parallel, just like a [PMOSFET](#). This helps in obtaining a high current carrying capacity for the device.

The equivalent circuit of the MCT is shown in the figure below.

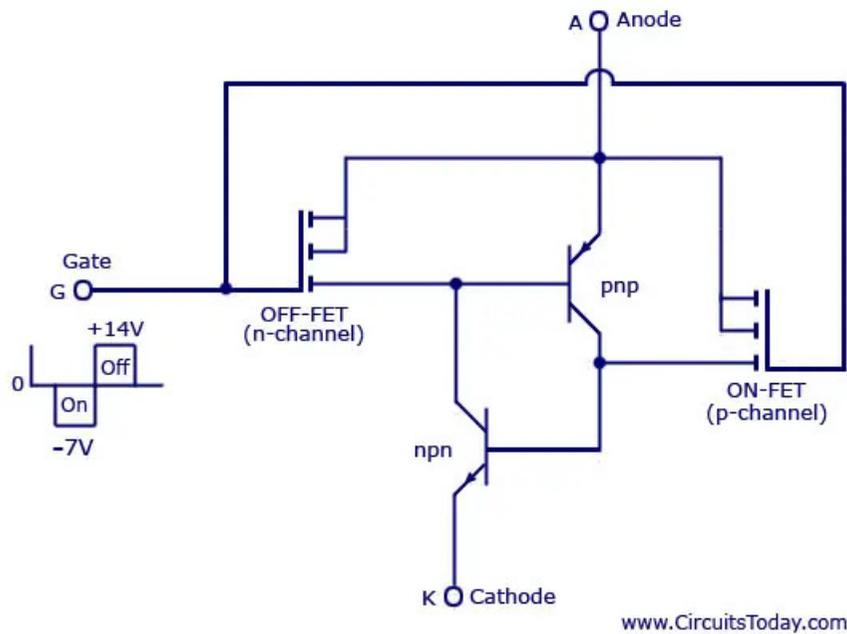
MOS-Controlled Thyristor (MCT) Equivalent Circuit



MOS Controlled Thyristor (MCT) Equivalent Circuit

It consists of an ON-FET, an OFF-FET and two transistors. The MOS structure of the MCT is represented in the equivalent circuit. It consists of one ON-FET, a p-channel MOSFET, and an OFF-FET. Both n-p-n and p-n-p transistors are joined together to represent the n-p-n-p structure of MCT. An n-channel MOSFET is represented by drawing the arrow towards the gate terminal. A p-channel MOSFET is indicated by drawing the arrow away from the gate terminal. The two transistors in the equivalent circuit indicate that there is regenerative feedback in the MCT just as it is an ordinary thyristor. The circuit symbol of MCT is shown below.

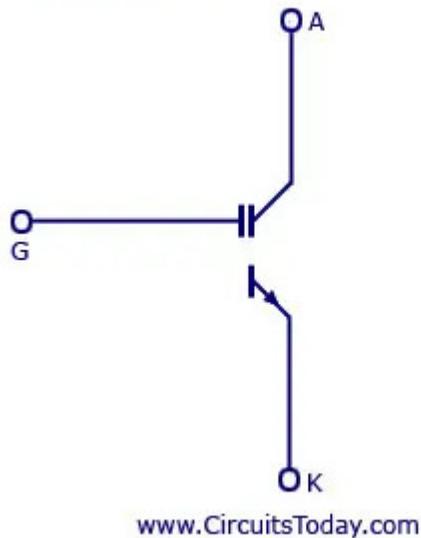MOS-Controlled Thyristor (MCT) Circuit Symbol



MOS-Controlled Thyristor (MCT) Circuit Symbol

Turning ON Process

The device is turned ON by a negative voltage pulse at the gate with respect to the anode. For turning ON MCT, gate is made negative with respect to anode by the voltage pulse between gate and anode. So, MCT must be initially forward biased, and then only a negative voltage be applied. With the application of this negative voltage pulse, ON-FET gets turned ON whereas OFF-FET is already OFF. With ON-FET ON, current begins to flow from anode A, through ON-FET and then as the base current and emitter of n-p-n transistor and then to cathode K. This turns on n-p-n transistor. This causes the collector current to flow in n-p-n transistor. As OFF FET is OFF, this collector current of npn transistor acts as the base current of p-n-p transistor. Subsequently, p-n-p transistor is also turned ON. If both the transistors are ON, regenerative action of the connection scheme takes place and the MCT is turned ON.

Turning OFF process

The device is turned OFF by applying a positive voltage pulse at the gate. The positive voltage pulse causes the OFF-FET to turn ON and ON-FET to turn OFF. After OFF-FET is turned ON, emitter based terminals of p-n-p transistor are short circuited by OFF-FET. So, now anode current begins to flow through OFF-FET and thus base current of p-n-p transistor begins to decrease. The device has the disadvantage of reverse voltage blocking capability.

Advantages of MCT

1. Low forward conduction drop

2. Fast TURN-ON and then OFF times
3. Low switching losses
4. High gate input impedance