



# Noise in OAs

[SLYT-051 + SLVA043 + AN-104 + AN-358]

- Noise factor

$$F = \frac{\text{SNR}_I}{\text{SNR}_O}$$

- Noise figure

$$(F): NF \text{ (dB)} = 10 \log(F).$$

$$F = \frac{\text{SNR}_I}{\text{SNR}_O} = \left[ \frac{\frac{S_I}{N_I}}{\frac{G \times S_I}{G(N_I + N_A)}} \right] = 1 + \frac{N_A}{N_I}$$

Note: these are powers, not intensities;  $G$  is the *power gain*

Figure 1. Non-inverting noise analysis diagram


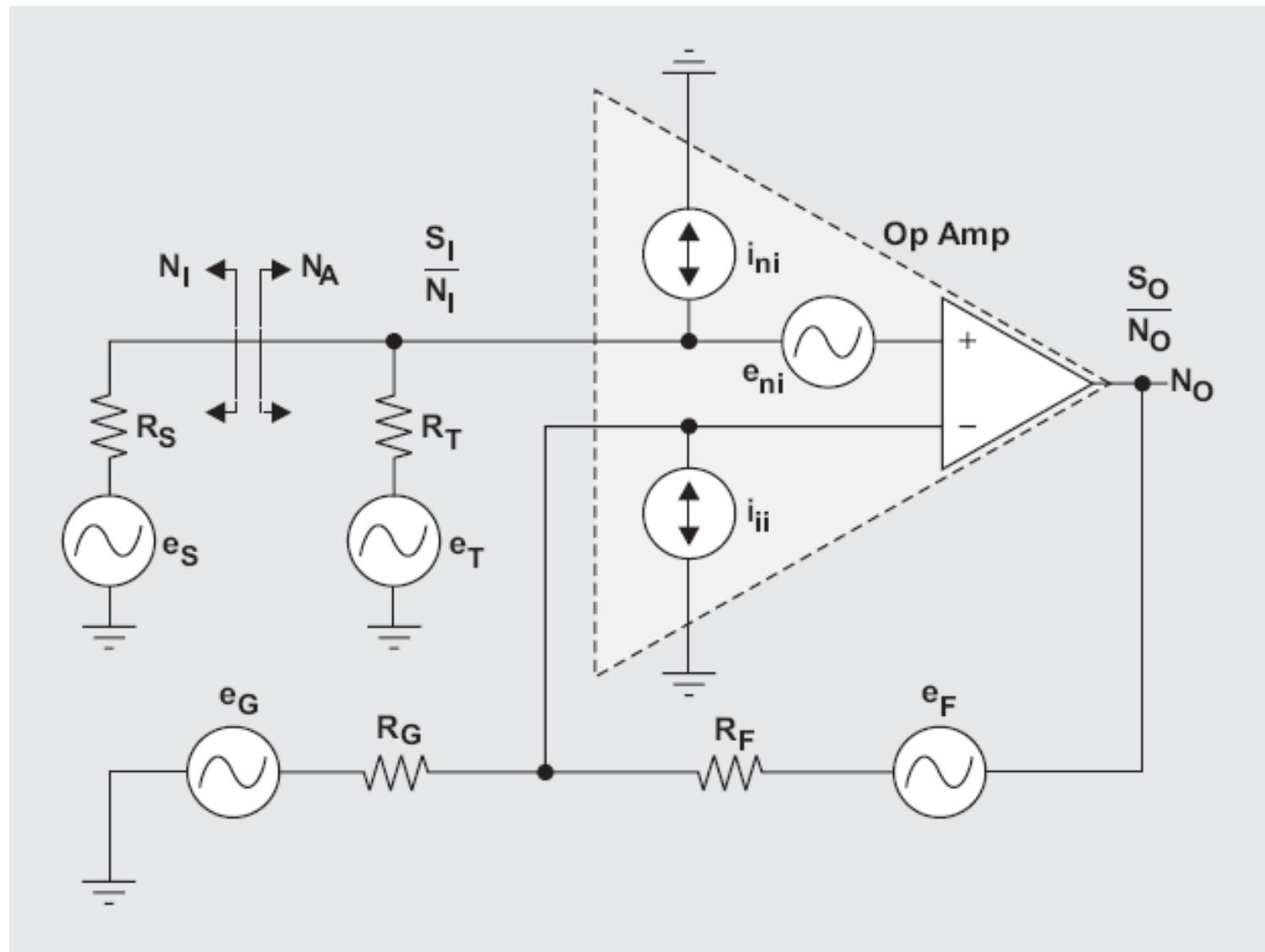


Figure 2. Inverting noise analysis diagram

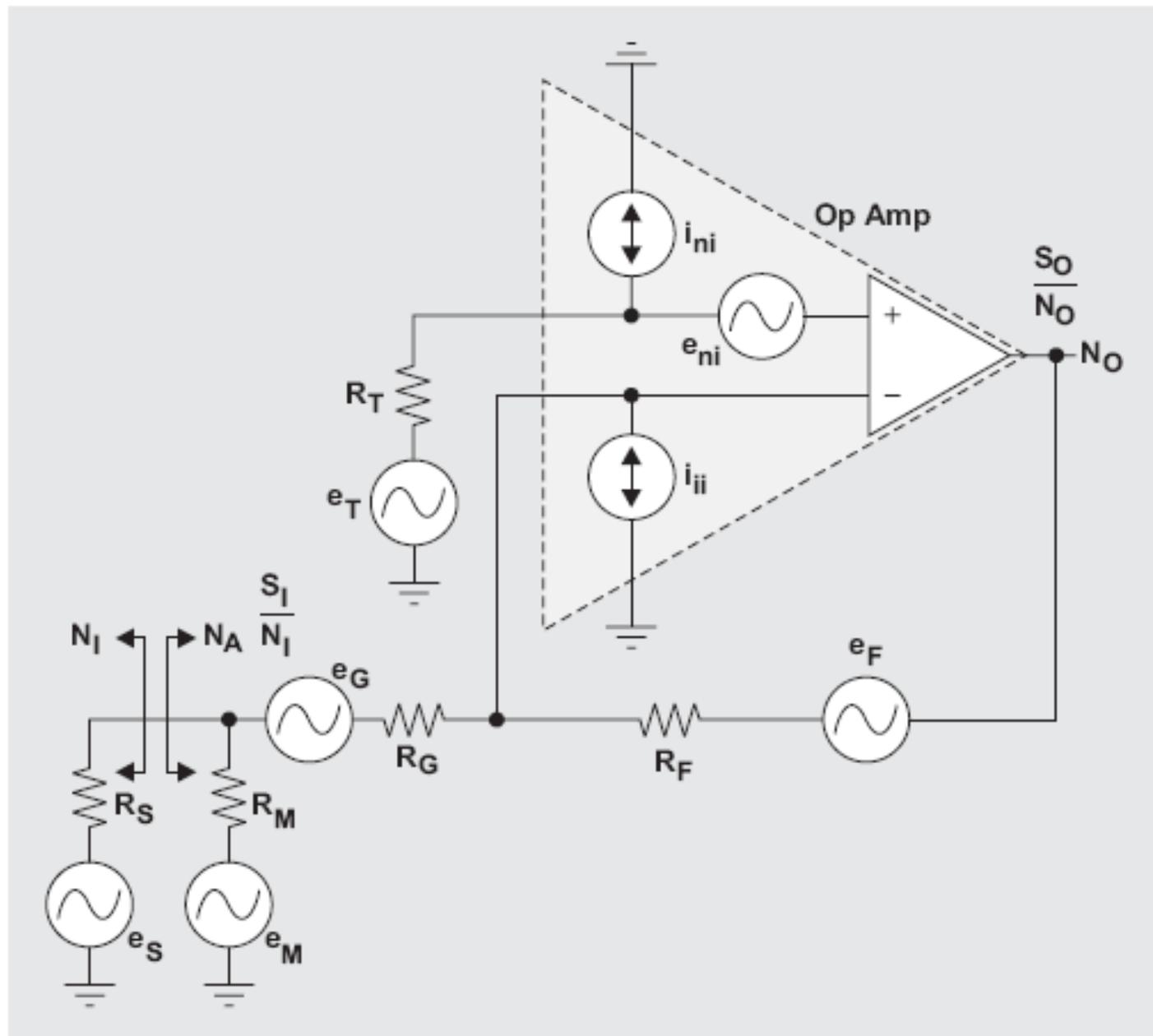

### Signal input noise ( $N_I$ ) terms

AMPLIFIER CONFIGURATION	NOISE SOURCE	NOISE CONTRIBUTION
Non-inverting	Source thermal noise	$4kTR_S \left( \frac{R_T}{R_S + R_T} \right)^2$
Inverting	Source thermal noise	$N_I = 4kTR_S \left[ \frac{R_M R_S}{R_S (R_M + R_G) + (R_M R_G)} \right]^2$ (1)

(1) no, the numerator is  $R_M R_G$

it comes out from the voltage divider

$$(R_M // R_G) / (R_M // R_G + R_S)$$

Device input noise ( $N_A$ ) terms

AMPLIFIER CONFIGURATION	NOISE SOURCE	NOISE CONTRIBUTION
Non-inverting	Op amp input-referred voltage noise	$e_{ni}^2$
	Op amp non-inverting input-referred current noise	$i_{ni}^2 \left( \frac{R_S R_T}{R_S + R_T} \right)^2$
	Op amp inverting input-referred current noise	$i_{ii}^2 \left( \frac{R_F R_G}{R_F + R_G} \right)^2$ (1)
	Termination resistor thermal noise voltage	$4kTR_T \left( \frac{R_S}{R_S + R_T} \right)^2$
	Gain resistor thermal noise voltage	$4kTR_G \left( \frac{R_F}{R_F + R_G} \right)^2$ (1)
	Feedback resistor thermal noise voltage	$4kTR_F \left( \frac{R_G}{R_F + R_G} \right)^2$ (1)

(1) from SLVA043A

Inverting	Op amp input-referred voltage noise	$e_{ni}^2 \left( \frac{R_G}{R_F} + \frac{R_G}{R_G + \frac{R_S R_M}{R_S + R_M}} \right)^2$
	Op amp non-inverting input-referred current noise	$i_{ni}^2 \left( \frac{R_T R_G}{R_F} + \frac{R_T R_G}{R_G + \frac{R_S R_M}{R_S + R_M}} \right)^2$
	Op amp inverting input-referred current noise	$i_{ii}^2 (R_G)^2$
	Non-inverting bias matching resistor thermal noise voltage	$4kTR_T \left( \frac{R_G}{R_F} + \frac{R_G}{R_G + \frac{R_S R_M}{R_S + R_M}} \right)^2$
	Gain resistor thermal noise voltage	$4kTR_G \left( \frac{R_G}{R_G + \frac{R_S R_M}{R_S + R_M}} \right)^2$
	Feedback resistor thermal noise voltage	$4kTR_F \left( \frac{R_G}{R_F} \right)^2$
	Inverting termination matching resistor thermal noise voltage	$4kTR_M \left[ \frac{R_S R_G}{R_M (R_S + R_G) + R_S R_G} \right]^2$



For the configuration as differential amp. See [SLVA043A](#)  
For the fully differential opamp see [SLYT051](#)