 




CFA3

[OA-13, AD_faq_ask23, OA-30, OA-07]

Understanding the loop gain [OA-13]




Hence, Loop Gain (LG) =
$$\frac{Z(s)}{R_f + R_i \left(1 + \frac{R_f}{R_g}\right)}$$

= $\frac{\text{internal forward transimpedance}}{\text{feedback transimpedance}}$

- CLC400: in nominal conditions
- $R_f=R_g=250 \Omega, A_v=2; R_i=50 \Omega$
 - $Z_t=250+50*2=350 \Omega \sim 50.9 \text{ dB}$

Z_t here is the name of the "old" Z_2

 - [or $R_f=40 \Omega \rightarrow Z_t=330$]




Understanding the loop gain [OA-13]

Where loop gain = 1 (red dot):


- $\arg(-Z) \sim -300$
- phase margin ~ 60 deg

CFA's are normally designed to work with at least that phase margin ->

it is advisable *not* to change Z_t

 

*

 

Controlling the loop gain

If a different A_v from the nominal one is need?

*Try to use the optimal feedback transimpedance Z_t^**

- Using the nominal values, compute Z_t^*

$$R_f + R_i (1 + R_f/R_g) = Z_t^*$$

- For the desired A_v , compute R_f

$$R_f = Z_t^* - R_i A_v$$

- and finally get R_g from

$$A_v = 1 + R_f/R_g$$

- e.g, for the CLC400, $Z_t^* = 250 + 50 * 2 = 350 \Omega$
- e.g, for the CLC406, $Z_t^* = 500 + 60 * 6 = 860 \Omega$

(from OA13)

TABLE 1. Comlinear Monolithic, Current Feedback, Amplifier Optimum Feedback Transimpedance and Operating Point Information

Part #	Design Point Information				Operating Current		comments
	A_v	R_f (Ω)	R_i (Ω)	Z_t^* (Ω)	I_c (mA)	I_c/I_{cc}	
CLC400	+2	250	40	330	.67	.045	
CLC401	+20	1500	50	2500	.52	.035	
CLC402	+2	250	16	282	.82	.055	
CLC404	+6	500	30	680	.87	.080	
CLC406	+6	500	60	860	.43	.09	
CLC409	+2	250	25	300	1.05	.08	
CLC410	+2	250	35	320	.74	.05	disable left open
CLC411	+2	301	50	400	.52	.05	disable left open
CLC414	+6	500	250	2000	.105	.05	each amplifier of quad
CLC415	+6	500	60	860	.43	.09	each amplifier of quad
CLC430	+2	750	60	870	.43	.04	disable left open
CLC500	+2	250	32	314	.82	.05	
CLC501	+20	1500	30	2100	.86	.05	see (Note 3)
CLC505	+6	1000	50	1300	.52	.06	$I_{cc} = 9.0\text{mA}$ $R_p = 33\text{k}\Omega$
CLC505	+6	1000	150	1900	.175	.06	$I_{cc} = 3.3\text{mA}$ $R_p = 33\text{k}\Omega$
CLC505	+6	1000	490	3950	.053	.06	$I_{cc} = 1.0\text{mA}$ $R_p = 33\text{k}\Omega$

Note 1: Power supplies at $\pm 5\text{V}$

Note 2: 25°C temperature assumed: yields $kT/q = .26\text{V}$

Note 3: CLC501 specification point at $A_v = +32$, $R_f = 1500\Omega$ Design point, however is at $A_v = +20$, $R_f = 1500\Omega$

Controlling the loop gain

This example: for the CLC 404

- nominal values are

$$A_V = +6$$

$$R_f = 500 \Omega$$

$$R_i = 30 \Omega$$

- so that ($A_V = 2, 6, 11$)

$$Z_t^* = 500 + 30 * 6 = 680 \Omega$$

(above): with fixed R_f

(below) with $Z_t = Z_t^*$: better!

 


FIGURE 4. Frequency Response vs. Gain for R_f Fixed = 500 Ω


 



FIGURE 5. Frequency Response vs. Gain for Fixed $Z_t = Z_t^* = 680 \Omega$

To drive a capacitive load [AD_faq/ask2, p. 2.9]

 - A capacitor on the output increases the phase -> possible instability.
- The easiest solution:
 - resistor in series




VFA / CFA comparison [OA-30]

 

0150141

FIGURE 5. Typical VFB Input Stage

 

01501412

FIGURE 7. Basic CFB Topology

VFA / CFA comparison [OA-30]

- Normally, the input stage of a VFB is a differential stage
 - > two equally biased, matched transistors -> error compensation ->
 - low input offset voltage V_{io}
 - matched input bias current I_b
 - high PSRR
 - good CMRR

Moreover, lower noise and feedback freedom

VFA / CFA comparison [OA-30]

- Normally, the CFA input stage is a push-pull stage -> an NPN and a PNP -> no matching ->
 - higher V_{io}
 - unmatched I_b
 - worse PSRR and CMRR
 - higher noise; limited feedback freedom

CFA

- No gain-bandwidth trade-off
- Often, the CFA is simpler (an input buffer, a gain stage and an output buffer) -> fewer stages -> faster
- f_{in} in C is not limited -> no slew rate limitation, apart from
 - saturation effects [AD_faq/ask1, p. 2.9]
 - transistor current gain degradation at high current levels [AN-NS92, p. 5.b.6]
 - capacitive effects


Some modern VFAs (e.g. AD9632) have similar characteristics

CFA

- Distortions are normally due to asymmetries and limited speed
 - complementary symmetry -> lower distortion
 - being faster, at high speed the loop gain is higher -> lower distortion

Application circuit guide

 - see OA-07
- E.g.: high pass: KRC (i.e. Sallen-Key)



CFA params modeled by the National SPICE models [OA-18]

■ DC EFFECTS

- V_{IO} , I_{BI} , I_{BN}
- Supply current vs. supply voltages
- Common mode input/output voltage range
- Load current from supplies
- CMRR

■ AC EFFECTS < 500 MHz

- Frequency response vs. gain & load
- Open loop gain & phase
- Noise
- Small signal input/output impedance

■ TIME DOMAIN

- Rise/fall times
- Slew rates

■ SPECIAL FEATURES (WHERE APPLICABLE)

- Output clamping
- Supply current adjustment
- Offset voltage adjust
- Disable/enable times
- External compensation

CFA parameters **not** modeled by the National SPICE models

- • Differential gain and phase
- • PSRR
- • Harmonic distortion
- • Fine scale settling performance
- • Thermal tail

LMH6714

- Suggested operation: $A_V=+2$, $R_f=300\ \Omega$
- see data sheets...
- $R_i \sim 180\ \Omega$
- slew rate: 1800 V/us
- improved replacement for CLC 400, 401, 402, 404, 406
- suggested R_f values are provided for different values of A_V (p. 9, figure 2)
- for gains > 5 it behaves as a GBP limited OA

LT1206 and LT 1210

- High output current drive capability (250 mA and 1.1 A, resp.)
- stable with large capacitive load (up to 10 nF)
- suggested values of R_F and R_G are provided for different gains (and loads and power supply)

AD8009

- Ultrahigh speed current feedback amplifier with a phenomenal 5,500 V/ μ s slew rate
- suggested R_F also depends on the IC package!