




Buck SMPS fundamentals

[TI_slva057]

Introduction

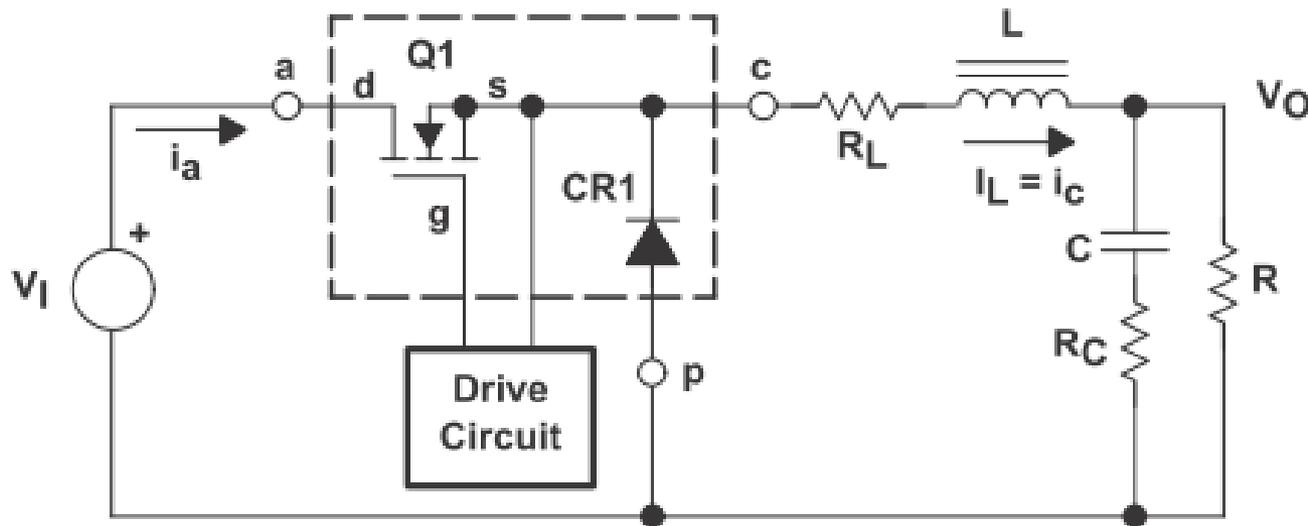- Simplified schematic of the buck power stage with a drive circuit block included. The power switch, $Q1$, here is an n-channel MOSFET.



- The diode, $CR1$, is usually called *catch diode*, or *freewheeling diode*
- The inductor, L , and capacitor, C , make up the output filter
- The capacitor ESR, R_C , (equivalent series resistance) and the inductor DC resistance, R_L , are included in the analysis

Buck Steady-State Mode Analysis

- A power stage can operate in continuous (CCM) or discontinuous (DCM) inductor current mode (see later)
 - continuous inductor current mode is characterized by current flowing continuously in the inductor
 - discontinuous inductor current mode is characterized by the inductor current being zero for a portion of the switching cycle
- Here, an n-channel power MOSFET is used
 - the advantage of using an n-channel FET is its lower $R_{DS(on)}$ but the drive circuit is more complicated because a floating drive is required
 - for the same die size, a p-channel FET has a higher $R_{DS(on)}$ but usually does not require a floating drive circuit
- Steady-state implies that the input voltage, output voltage, output load current, and duty-cycle are fixed and not varying

Buck Steady-State CCM Analysis


- In CCM, the Buck power stage assumes two states per switching cycle

Note the


- active (a),
- passive (p), and
- common (c)

nodes: they'll be used later

ON State

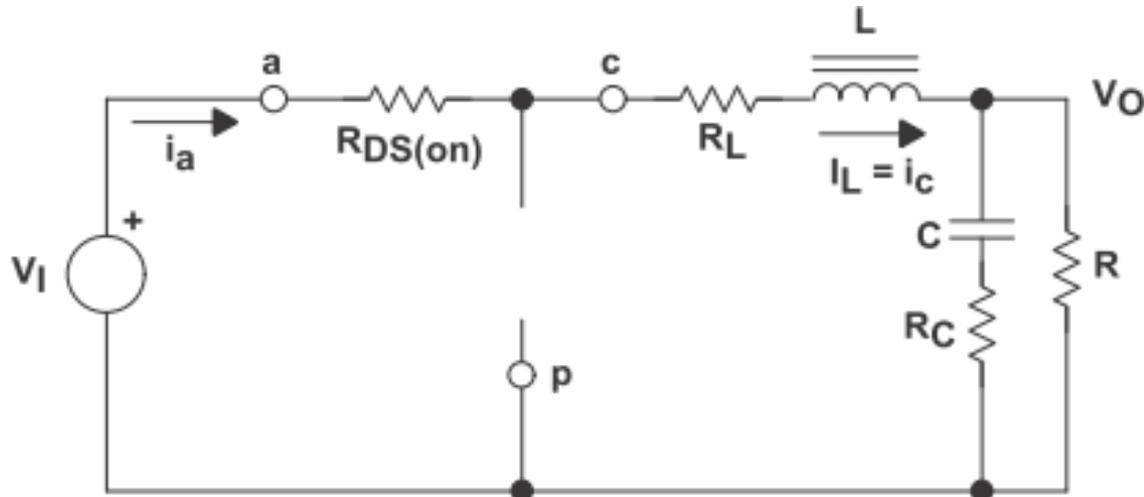


OFF State

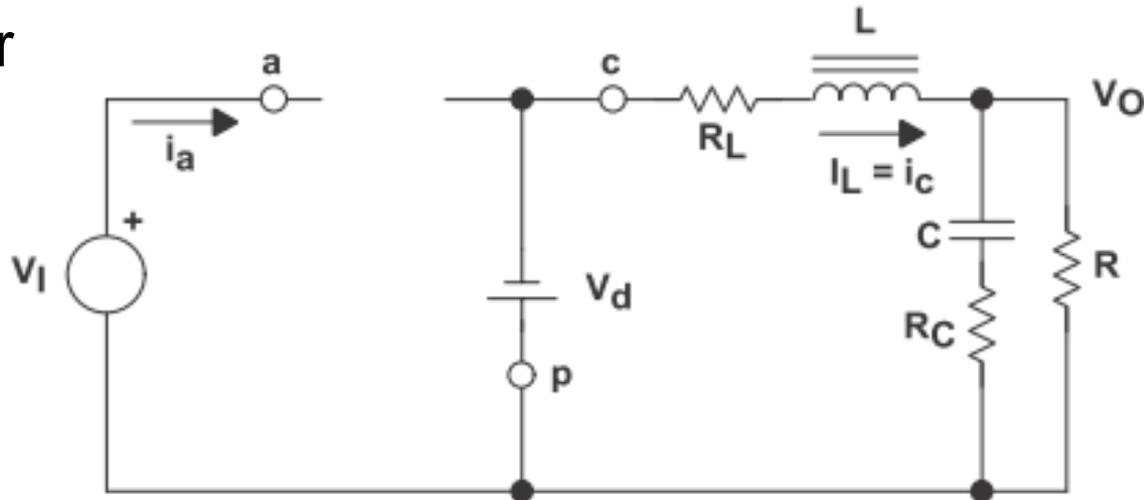

Buck Steady-State CCM Analysis


Waveforms in CCM

$$D = T_{ON} / T_S$$

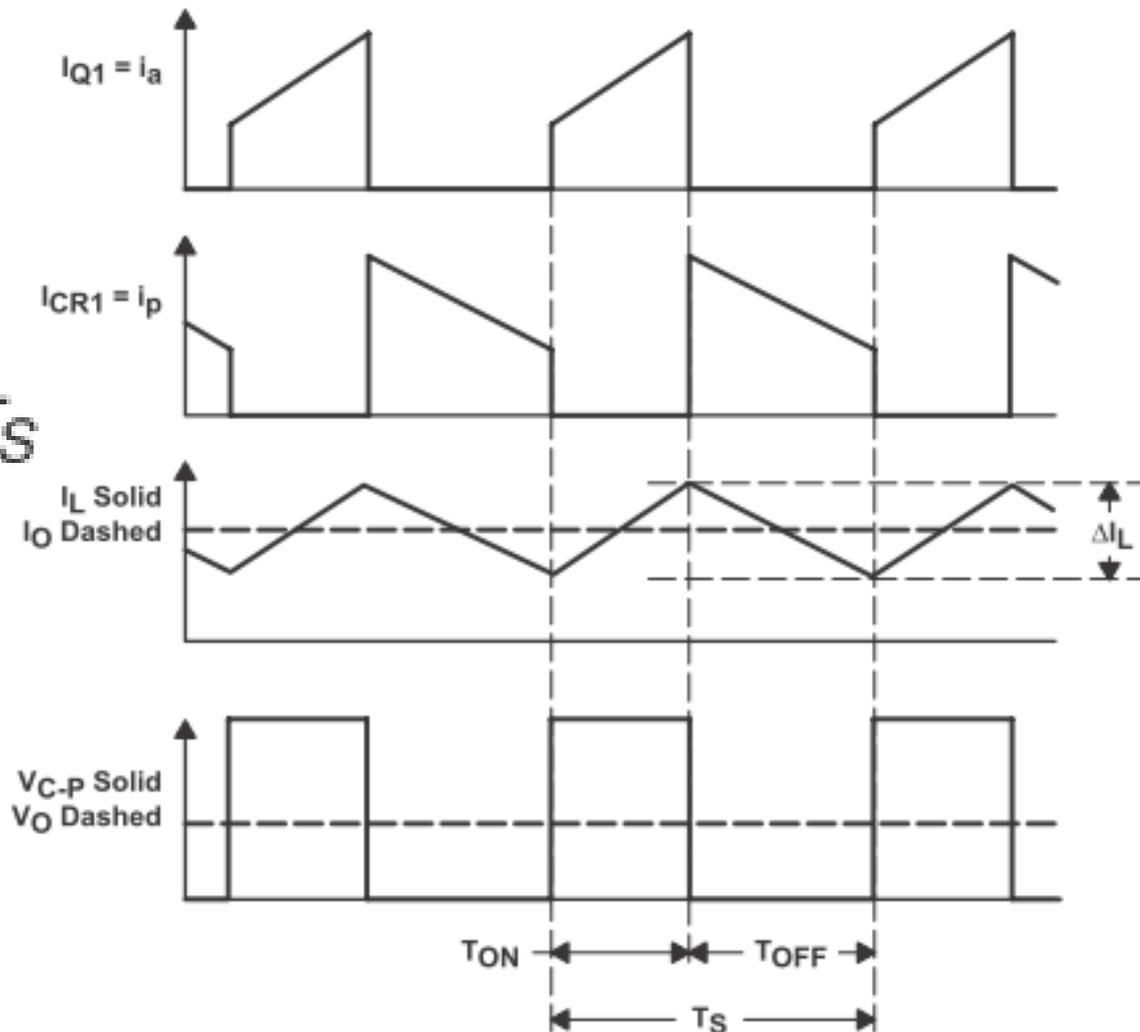


Buck Steady-State DCM Analysis

- If the output load current is reduced below the critical current level, the inductor current will be zero for a portion of the switching cycle
 - in CCM, the peak to peak amplitude of the ripple current does not change with output load current
 - if the inductor current attempts to fall below zero, it just stops at zero because of the diode
- A power stage operating in DCM has three unique states during each switching cycle (ON, OFF and IDLE (D_3T_s))

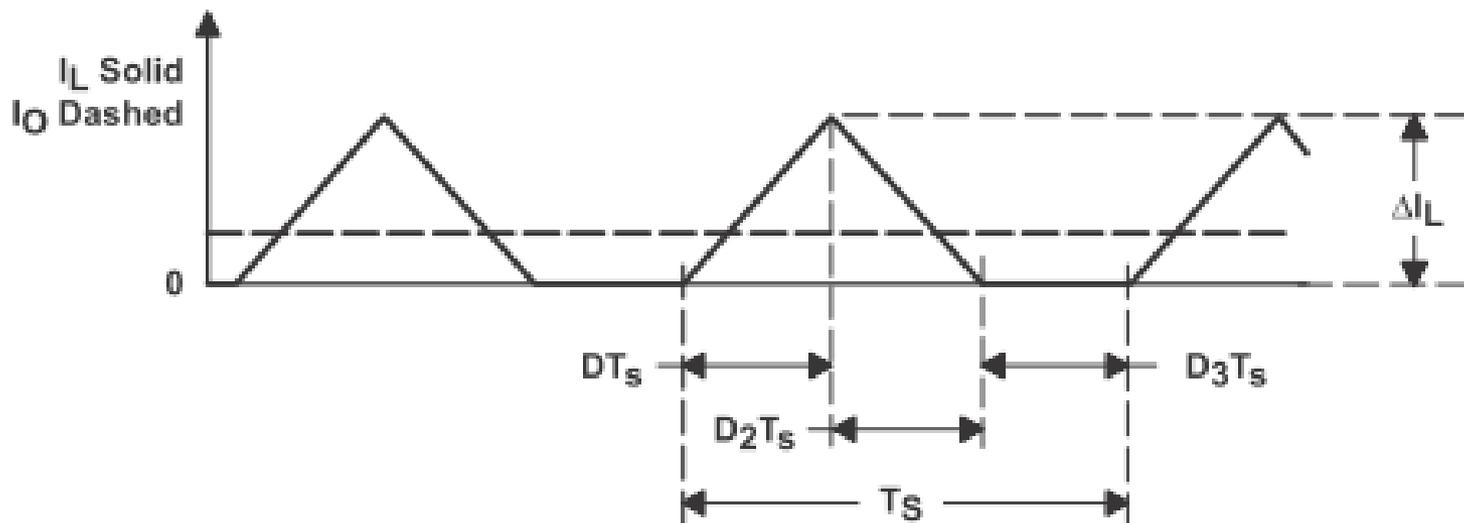

Buck Steady-State DCM Analysis

Waveforms:

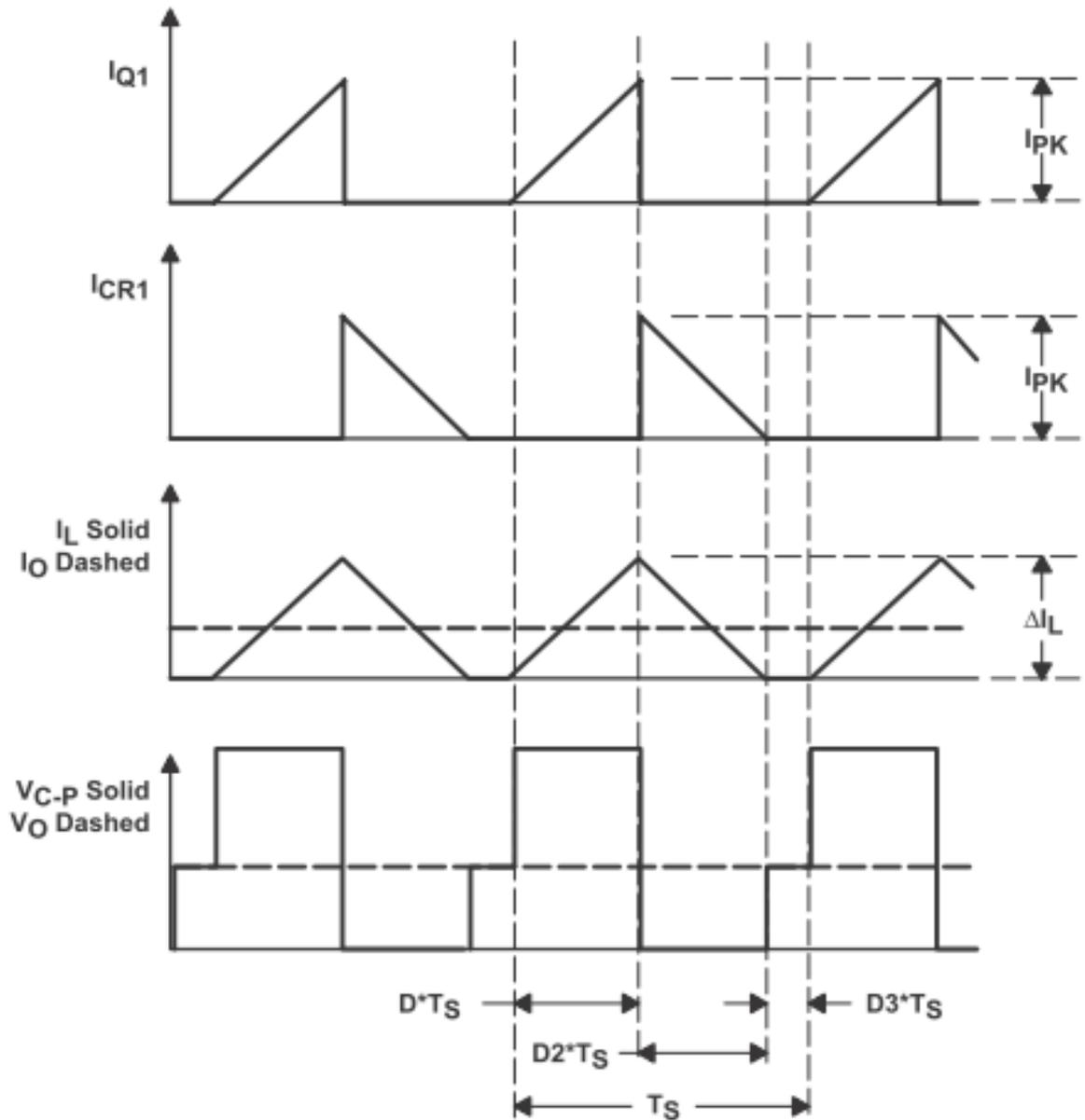


CCM and DCM

- Buck power stage are rarely operated in DCM in normal situations,
 - but DCM will occur anytime the load current is below the critical level
- A buck power stage can be designed to operate in CCM for load currents above a certain level
 - usually 5% to 10% of full load

Synchronous Buck Power Stage

- The buck converters seen up to now are *non-synchronous*
- In *synchronous* converters, an active switch such as another power MOSFET, Q2 in this example, replaces the diode
 - this FET is then selected so that its ON-voltage drop is less than the forward drop of the diode
- either the drive circuit or the controller must insure that both FETs are not on simultaneously
 - a small amount of deadtime is necessary
- it always operates in CCM because current can reverse in Q2

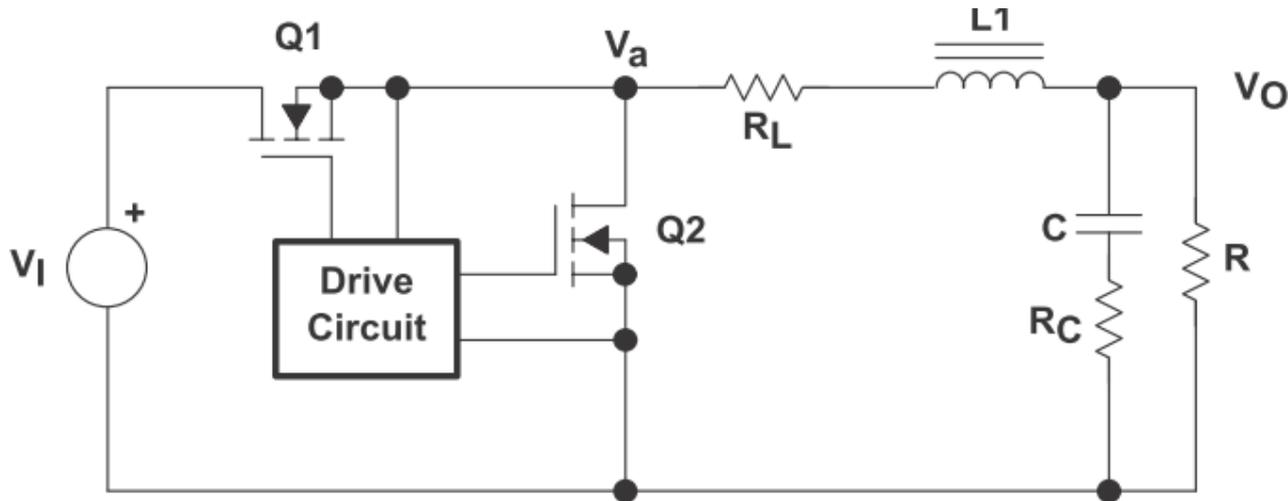

Buck Power Stages: other categories

Buck switching solutions include

- *power modules*: integrated FETs and inductor
- *converters (regulators)*: integrated FET or FETs and external inductor
- *controllers*: external FETs and inductors

The compensation of the control loop may be

- *internal*
- *external*

