 


Basic calculations for buck SMPS design

[TI_slva477b, TI_slva034a,
TI_slvaeq9]

Basic Configuration of a Buck Converter



- The following four parameters are needed to calculate the power stage:
 - Input voltage range: $V_{IN(min)}$ and $V_{IN(max)}$
 - Nominal output voltage: V_{OUT}
 - Maximum output current: $I_{OUT(max)}$
 - Integrated circuit used to build the buck converter

Calculate the Maximum Switch Current

- *Maximum switch current* duty cycle:

$$D_m = \frac{V_{OUT}}{V_{IN(max)} \times \eta}$$

with η = efficiency of the converter, e.g., estimated 90%

- Inductor ripple current:

$$\text{Inductor Ripple Current: } \Delta I_L = \frac{(V_{IN(max)} - V_{OUT}) \times D_m}{f_S \times L}$$

with D_m as above, and L taken from datasheet, or computed (see later)

- Verify that the IC or FET can deliver the maximum switch current

$$I_{SW(max)} = \frac{\Delta I_L}{2} + I_{OUT(max)}$$

Inductor selection

- Data sheets often give a range of recommended inductor values
 - if this is the case, choose an inductor from this range
 - the higher the inductor value, the higher the maximum output current (because of the reduced ripple current)
 - the lower the inductor value, the smaller the solution size
 - the inductor must always have a higher current rating than the maximum switch current
- Otherwise, using $D=V_{OUT}/V_{IN}$

$$L = \frac{V_{OUT} \times (V_{IN} - V_{OUT})}{\Delta I_L \times f_S \times V_{IN}}$$

with V_{IN} typical input voltage and ΔI_L estimated with

$$\Delta I_L = (0.2 \text{ to } 0.4) \times I_{OUT(max)}$$

Diode selection

- To reduce losses, use Schottky diodes
- Forward current rating: maximum average output current

$$I_F = I_{OUT(max)} \times (1 - D_m)$$

with D_m as above

- Schottky diodes have a much higher peak current rating than average rating -> peak current in the system is not a problem
- Power dissipation of the diode:


$$P_D = I_F \times V_F$$

Output Voltage Setting

- Almost all converters set the output voltage with a resistive divider network
 - which is integrated if they are fixed output voltage converters
- Current through the resistive divider needs to be at least 100 times as big as the feedback bias current (from data sheet)
- R_1 and R_2 must give

$$V_{FB} = R_2 / (R_1 + R_2) V_{OUT}$$

with V_{FB} from data sheet

 

Input Capacitor Selection

- Minimum value for the input capacitor is normally given in the data sheet
 - necessary to stabilize the input voltage due to the peak current requirement of the switching power supply
- Use low-equivalent series resistance (ESR) ceramic capacitors
- The value can be increased if the input voltage is noisy

Output Capacitor Selection

- Use low-ESR capacitors to minimize the ripple on the output voltage
- *Externally compensated converters:*
 - any capacitor value above the recommended minimum in the data sheet can be used, but
 - the compensation has to be adjusted for the used output capacitance.
- *Internally compensated converters:*
 - the recommended inductor and capacitor values must be used, or
 - the recommendations in the data sheet for adjusting the output capacitors to the application in the data sheet must be followed for the ratio of $L \times C$

Output Capacitor Selection: external compensation

- The following equations can be used to adjust the output capacitor values for a desired output voltage ripple

$$C_{\text{OUT}(\text{min})} = \frac{\Delta I_L}{8 \times f_S \times \Delta V_{\text{OUT}}}$$

$C_{\text{OUT}(\text{min})}$ = minimum output capacitance

ΔI_L = estimated inductor ripple current

f_S = minimum switching frequency of the converter

ΔV_{OUT} = desired output voltage ripple

- The ESR of the output capacitor adds some more ripple:

$$\Delta V_{\text{OUT}(\text{ESR})} = \text{ESR} \times \Delta I_L$$

Output Capacitor Selection: external compensation

- Often the selection of the output capacitor is not driven by the steady-state ripple, but by the output transient response
 - the necessary output capacitance for a desired maximum overshoot can be calculated with

$$C_{\text{OUT}(\text{min}),\text{OS}} = \frac{\Delta I_{\text{OUT}}^2 \times L}{2 \times V_{\text{OUT}} \times V_{\text{OS}}}$$

$C_{\text{OUT}(\text{min}),\text{OS}}$ = minimum output capacitance for a desired overshoot

ΔI_{OUT} = maximum output current change in the application

V_{OUT} = desired output voltage


V_{OS} = desired output voltage change due to the overshoot

Power dissipation and efficiency

- There are several sources of loss

$$P_{\text{total_loss}} = P_{\text{switches}} + P_{\text{inductor}} + P_{\text{capacitors}} + P_{\text{other}}$$
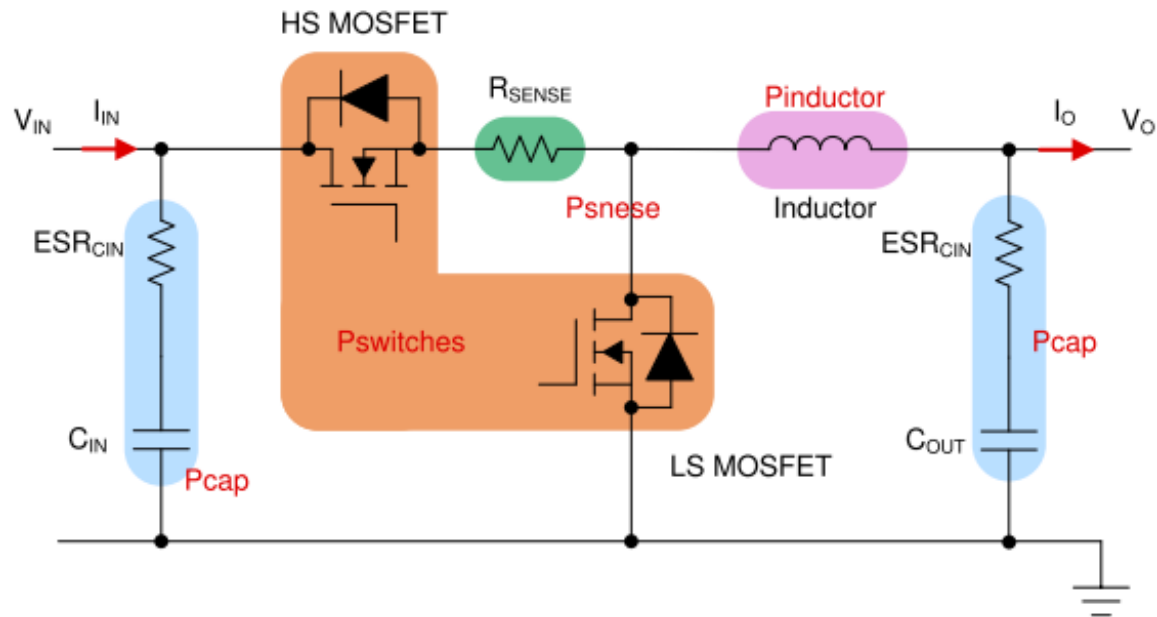
$$\eta = \frac{V_o I_o}{V_o I_o + P_{\text{total_loss}}} \times 100\%$$





Power dissipation and efficiency

Switch losses

- During t_2 and t_3 , I_{DS} and V_{DS} are not zero, so the switching loss is caused when MOSFET turns on and turns off

$$P_D = 0.5 \times V_I \times I_O \times t_{r+f} \times f_s$$

  with $t_{r+f} = t_r + t_f =$ total (turn-on and turn-off) FET switching time
with $t_r = t_2 + t_3$ (figure on the left), $t_f = t_3 + t_2$ (figure on the right)



Power dissipation and efficiency


Power dissipation, which includes both conduction and switching losses, can be approximated with

$$P_D = I_O^2 \times r_{DS(on)} \times D + 0.5 \times V_I \times I_O \times t_{r+f} \times f_s$$

More precise calculations, which include

- switching losses
- conduction losses (due to $r_{DS(on)}$)
- gate drive losses
- FET output capacitance losses (charge and discharge)
- inductor losses (due to ESR and core material)
- input and output capacitors losses (due to ESRs)
- sense resistor losses

can be found in *TI_slvaeq9*

 

SW tools

Some (often proprietary) tools do exist to help in the design:

- Linear Technology LTpowerCAD
 - free download at www.linear.com/LTpowerCAD
 - ready for LTspice simulation
- STM eDesignSuite
 - https://eds.st.com/console/#/app/dcdc/ic_dcdc_catalogs/filter/%5B%5D/grid